

PyZX: Quantum circuit optimization using the ZX-calculus

Aleks Kissinger

`aleks@cs.ru.nl`

John van de Wetering

`john@vdwetering.name`

Institute for Computing and Information Sciences
Radboud University Nijmegen

December 17, 2018

Introduction

- ▶ In fault-tolerant quantum computing, Clifford gates are cheap.

Introduction

- ▶ In fault-tolerant quantum computing, Clifford gates are cheap.
- ▶ But to achieve universal QC we need other gates.

Introduction

- ▶ In fault-tolerant quantum computing, Clifford gates are cheap.
- ▶ But to achieve universal QC we need other gates.
- ▶ Most commonly $T = R_Z(\pi/4)$.

Introduction

- ▶ In fault-tolerant quantum computing, Clifford gates are cheap.
- ▶ But to achieve universal QC we need other gates.
- ▶ Most commonly $T = R_Z(\pi/4)$.
- ▶ T gates are far more expensive than Clifford gates.

Introduction

- ▶ In fault-tolerant quantum computing, Clifford gates are cheap.
- ▶ But to achieve universal QC we need other gates.
- ▶ Most commonly $T = R_Z(\pi/4)$.
- ▶ T gates are far more expensive than Clifford gates.
- ▶ So:
Optimizing fault tolerant QC means optimizing T-count.

T-count optimization

Finding optimal T-count is NP-hard,
so we need heuristics.


T-count optimization

Finding optimal T-count is NP-hard,
so we need heuristics.

Existing heuristics fall basically in two categories.

Method 1: Commutation and Cancellation

Adjacent T gates become Clifford:

 

Method 1: Commutation and Cancellation

Adjacent T gates become Clifford:

$$\begin{array}{c} \text{---} \boxed{\text{T}^\dagger} \text{---} \boxed{\text{T}} \text{---} \\ \text{---} \boxed{\text{T}} \text{---} \boxed{\text{T}} \text{---} \end{array} = \begin{array}{c} \text{-----} \\ \text{---} \boxed{\text{S}} \text{---} \end{array}$$

⇒ By making T gates adjacent, we can decrease T count.

Method 1: Commutation and Cancellation

Adjacent T gates become Clifford:


$$\begin{array}{c} \text{---} \boxed{T^\dagger} \text{---} \boxed{T} \text{---} \\ \text{---} \boxed{T} \text{---} \boxed{T} \text{---} \end{array} = \begin{array}{c} \text{-----} \\ \text{---} \boxed{S} \text{---} \end{array}$$

⇒ By making T gates adjacent, we can decrease T count.


$$\begin{array}{c} \text{---} \boxed{T} \text{---} \bullet \text{---} \\ \text{---} \oplus \text{---} \end{array} = \begin{array}{c} \text{---} \bullet \text{---} \boxed{T} \text{---} \\ \text{---} \oplus \text{---} \end{array}$$
$$\begin{array}{c} \text{---} \bullet \text{---} \bullet \text{---} \\ \text{---} \oplus \text{---} \boxed{T} \text{---} \oplus \text{---} \boxed{T} \text{---} \oplus \text{---} \end{array} = \begin{array}{c} \text{---} \bullet \text{---} \bullet \text{---} \\ \text{---} \oplus \text{---} \boxed{T} \text{---} \oplus \text{---} \boxed{T} \text{---} \end{array}$$

Method 1: Commutation and Cancellation

Adjacent T gates become Clifford:

 

 ⇒ By making T gates adjacent, we can decrease T count.



And loads more...

Method 2: Phase Polynomials

Circuits built out of CNOT and T gates can be written as

$$U|\mathbf{x}\rangle = e^{i\frac{\pi}{4}g(\mathbf{x})} |f_1(\mathbf{x}), \dots, f_n(\mathbf{x})\rangle$$

where $\mathbf{x} \in \mathbb{Z}_2^n$ is a binary vector,

$g : \mathbb{Z}_2^n \rightarrow \mathbb{Z}_8$ is a polynomial and

$f_i : \mathbb{Z}_2^n \rightarrow \mathbb{Z}_2$ are \mathbb{Z}_2 -linear functions.

Method 2: Phase Polynomials

Circuits built out of CNOT and T gates can be written as

$$U|\mathbf{x}\rangle = e^{i\frac{\pi}{4}g(\mathbf{x})} |f_1(\mathbf{x}), \dots, f_n(\mathbf{x})\rangle$$

where $\mathbf{x} \in \mathbb{Z}_2^n$ is a binary vector,

$g : \mathbb{Z}_2^n \rightarrow \mathbb{Z}_8$ is a polynomial and

$f_i : \mathbb{Z}_2^n \rightarrow \mathbb{Z}_2$ are \mathbb{Z}_2 -linear functions.

\Rightarrow Using this translation, we can make interesting simplifications


Method 2: Phase Polynomials

Circuits built out of CNOT and T gates can be written as

$$U|\mathbf{x}\rangle = e^{i\frac{\pi}{4}g(\mathbf{x})} |f_1(\mathbf{x}), \dots, f_n(\mathbf{x})\rangle$$

where $\mathbf{x} \in \mathbb{Z}_2^n$ is a binary vector,
 $g : \mathbb{Z}_2^n \rightarrow \mathbb{Z}_8$ is a polynomial and
 $f_i : \mathbb{Z}_2^n \rightarrow \mathbb{Z}_2$ are \mathbb{Z}_2 -linear functions.

 \Rightarrow Using this translation, we can make interesting simplifications



(but optimal T-count finding still seems to be in NP)

Limitations

Using commutation, cancellation and phase polynomials,
a lot of progress can be made...

Limitations

Using commutation, cancellation and phase polynomials,
a lot of progress can be made...

...but there is an obvious limitation:

Limitations

Using commutation, cancellation and phase polynomials,
a lot of progress can be made...

...but there is an obvious limitation:

These methods never stray from the circuit model

Limitations

Using commutation, cancellation and phase polynomials,
a lot of progress can be made...


...but there is an obvious limitation:


These methods never stray from the circuit model

Enter the ZX-calculus

ZX-diagrams


- ▶ ZX-diagrams consist of two types of maps

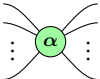
- ▶ Z-spiders  $:= |0 \cdots 0 \rangle \langle 0 \cdots 0| + e^{i\alpha} |1 \cdots 1 \rangle \langle 1 \cdots 1|$

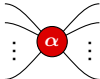- ▶ X-spiders  $:= |+\cdots+\rangle \langle +\cdots+| + e^{i\alpha} |-\cdots-\rangle \langle -\cdots-|$

ZX-diagrams

- ZX-diagrams consist of two types of maps

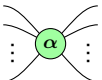- Z-spiders  $:= |0 \cdots 0 \rangle \langle 0 \cdots 0| + e^{i\alpha} |1 \cdots 1 \rangle \langle 1 \cdots 1|$

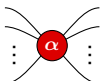
- X-spiders  $:= |+\cdots+\rangle \langle +\cdots+| + e^{i\alpha} |-\cdots-\rangle \langle -\cdots-|$


- By wiring these together, we can make arbitrary linear maps between qubits. For instance:

$$\begin{aligned}
 \text{H} &= \text{---} \square \text{---} = \text{---} \left(\text{---} \overset{\pi}{\underset{-}{\circ}} \text{---} \overset{\pi}{\underset{-}{\circ}} \text{---} \overset{\pi}{\underset{-}{\circ}} \text{---} \right) \text{---} & \text{T} &= \text{---} \overset{\pi}{\underset{4}{\circ}} \text{---} \\
 \text{CNOT} &= \text{---} \overset{\circ}{\underset{\circ}{\text{---}}} \text{---} & \text{CZ} &= \text{---} \overset{\square}{\underset{\square}{\text{---}}} \text{---}
 \end{aligned}$$

ZX-diagrams

- ZX-diagrams consist of two types of maps

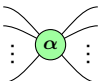- Z-spiders  $:= |0 \cdots 0 \rangle \langle 0 \cdots 0| + e^{i\alpha} |1 \cdots 1 \rangle \langle 1 \cdots 1|$

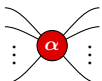- X-spiders  $:= |+\cdots+\rangle \langle +\cdots+| + e^{i\alpha} |-\cdots-\rangle \langle -\cdots-|$


- By wiring these together, we can make arbitrary linear maps between qubits. For instance:

$$H = \text{---} \square \text{---} = \text{---} \left(\text{---} \overset{\pi}{\underset{-}{2}} \text{---} \overset{\pi}{\underset{-}{2}} \text{---} \overset{\pi}{\underset{-}{2}} \text{---} \right) \text{---} \quad T = \text{---} \left(\overset{\pi}{4} \right) \text{---}$$

$$\text{CNOT} = \begin{array}{c} \text{---} \overset{\pi}{\underset{-}{2}} \text{---} \\ | \\ \text{---} \overset{\pi}{\underset{-}{2}} \text{---} \end{array} \quad \text{CZ} = \begin{array}{c} \text{---} \overset{\pi}{\underset{-}{2}} \text{---} \\ \square \\ \text{---} \overset{\pi}{\underset{-}{2}} \text{---} \end{array}$$

$$\text{But also: GHZ} = \text{---} \left(\overset{\pi}{\underset{-}{2}} \right) \text{---} \quad T \text{ magic state} = \text{---} \left(\overset{\pi}{4} \right) \text{---}$$

ZX-calculus

 

$$\alpha, \beta \in [0, 2\pi], a \in \{0, 1\}$$

Circuit optimization with the ZX-calculus

- ▶ Write your circuit as a ZX-diagram.

Circuit optimization with the ZX-calculus


- ▶ Write your circuit as a ZX-diagram.
- ▶ Apply rewrite rules to simplify it.

Circuit optimization with the ZX-calculus

- ▶ Write your circuit as a ZX-diagram.
- ▶ Apply rewrite rules to simplify it.
- ▶ Turn the resulting diagram back into a circuit.


First steps: graph-like ZX-diagrams

 - ▶ First turn all X-spiders into Z-spiders:



First steps: graph-like ZX-diagrams

 
- ▶ First turn all X-spiders into Z-spiders:





- ▶ Cancel all double Hadamards:  = .

First steps: graph-like ZX-diagrams

 
- ▶ First turn all X-spiders into Z-spiders:



- ▶ Cancel all double Hadamards:  = .
- ▶ Fuse all adjacent spiders.

First steps: graph-like ZX-diagrams

 
- ▶ First turn all X-spiders into Z-spiders:



- ▶ Cancel all double Hadamards:  = .


- ▶ Fuse all adjacent spiders.

- ▶ Cancel parallel connections:

 

First steps: graph-like ZX-diagrams

 
- ▶ First turn all X-spiders into Z-spiders:




- ▶ Cancel all double Hadamards:  = .

- ▶ Fuse all adjacent spiders.


- ▶ Cancel parallel connections:

 


- ▶ Use new notation:

 


Example

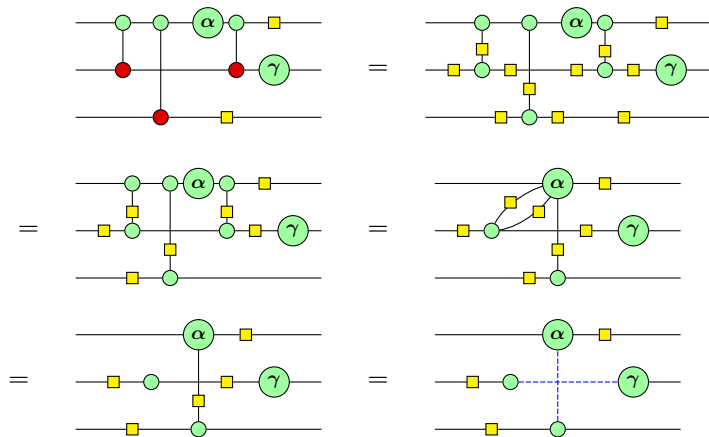


More involved example

 


=

 

More involved example

 


=

 

We call these diagrams *graph-like*.



More involved example

 

We call these diagrams *graph-like*.

To simplify these diagrams, we want to remove as many interior vertices as possible.

Local complementation and pivoting

  

Simplification so far

- ▶ Convert diagram into graph-like diagram.

Simplification so far


- ▶ Convert diagram into graph-like diagram.
- ▶ Remove all internal $\pm\pi/2$ spiders by local complementation.

Simplification so far

- ▶ Convert diagram into graph-like diagram.
- ▶ Remove all internal $\pm\pi/2$ spiders by local complementation.
- ▶ Remove all connected internal $a\pi$ spiders by pivoting.


Simplification so far

 - ▶ Convert diagram into graph-like diagram.
- ▶ Remove all internal $\pm\pi/2$ spiders by local complementation.
- ▶ Remove all connected internal $a\pi$ spiders by pivoting.
- ▶ Remove internal $a\pi$ spider connected to boundary by unfusing and pivoting:



Simplification so far

 
- ▶ Convert diagram into graph-like diagram.
- ▶ Remove all internal $\pm\pi/2$ spiders by local complementation.
- ▶ Remove all connected internal $a\pi$ spiders by pivoting.
- ▶ Remove internal $a\pi$ spider connected to boundary by unfusing and pivoting:




- ▶ If the original diagram was Clifford, then the simplified diagram has no internal spiders

Clifford example


Recall the example Clifford diagram:

 

Clifford+T example

 


Clifford+T example

 

Question: How do we turn this into a circuit.

Clifford+T example

 

Question: How do we turn this into a circuit.

Answer: We use the fact that it has a *gFlow*.

Informally, a gFlow associates an 'arrow of time' with a graph.
Circuits have a gFlow.

gFlow

Informally, a gFlow associates an 'arrow of time' with a graph.
Circuits have a gFlow.

Proposition

Local complementation and pivoting preserve gFlow

Informally, a gFlow associates an 'arrow of time' with a graph.
Circuits have a gFlow.

Proposition

Local complementation and pivoting preserve gFlow

Theorem

There is an efficient procedure that transforms a ZX-diagram with a gFlow into a circuit.

The simplification procedure

- ▶ We indeed have a circuit-to-circuit simplification procedure using the ZX-calculus.
- ▶ It reduces Clifford circuits to a quasi normal-form.

The simplification procedure


- ▶ We indeed have a circuit-to-circuit simplification procedure using the ZX-calculus.
- ▶ It reduces Clifford circuits to a quasi normal-form.
- ▶ But: T gates never get removed by lcomp and pivoting.

The simplification procedure

- ▶ We indeed have a circuit-to-circuit simplification procedure using the ZX-calculus.
- ▶ It reduces Clifford circuits to a quasi normal-form.
- ▶ But: T gates never get removed by lcomp and pivoting.
- ▶ So:
To do significant T-count optimization, we need to do better.


Gadgetization

 We turn all non-Clifford spiders into *phase gadgets*:



Gadgetization

 
We turn all non-Clifford spiders into *phase gadgets*:



This makes the base of the gadget available for pivoting.

 
Example: Gadgetization and pivoting

After the first round of simplifications:




 Example: Gadgetization and pivoting

After the first round of simplifications:




After gadgetization:

 


 Example: Gadgetization and pivoting


After the first round of simplifications:



After gadgetization:

 


After pivots/lcomps:

 

Final step: phase gadget fusion

 Whenever phase gadgets have the same set of neighbours, they can fuse:



Spider fusion + Local complementation + Pivoting
+ Gadgetization + Gadget fusion
=
State-of-the-art T-count optimization

Circuit extraction

Problem: We still need to get a circuit out of the diagram.

Circuit extraction

Problem: We still need to get a circuit out of the diagram.

The good news: We have 'heuristics' that always seem to work.

Circuit extraction

Problem: We still need to get a circuit out of the diagram.

The good news: We have 'heuristics' that always seem to work.

The bad news: We don't know why.

Demonstration of PyZX

Conclusion and future work

The Takeaway:
The ZX-calculus is very useful for
T-count optimization

Conclusion and future work

The Takeaway:
The ZX-calculus is very useful for
T-count optimization

Open problems:

- ▶ Why does our circuit extraction work?

Conclusion and future work

The Takeaway:
The ZX-calculus is very useful for
T-count optimization

Open problems:

- ▶ Why does our circuit extraction work?
- ▶ How to use phase-polynomial methods on ZX-diagrams?

Conclusion and future work

The Takeaway:
The ZX-calculus is very useful for
T-count optimization

Open problems:

- ▶ Why does our circuit extraction work?
- ▶ How to use phase-polynomial methods on ZX-diagrams?
- ▶ Is the ZH-calculus useful?

Thank you for your attention